
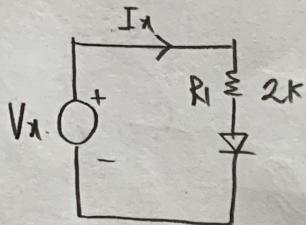


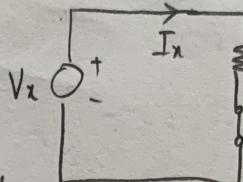2.18 consider circuit where $I_s = 2 \times 10^{-15} A$. calculate V_{D1} and I_x for $V_x = 0.5 V, 0.8 V, 1V$ and $1.2 V$. Note that V_{D1} changes little for $V_x \geq 0.8V$



기본적으로 $V_x > 0.8V$ 일 때 $V_x > V_{D,ON}$ 은 넘어서 전류가 forward bias이다.

그로,



이 두 식을 통해 값을 얻을 수 있다.

- $I_x = I_s \cdot \exp\left(\frac{V_D}{V_T} - 1\right)$ 이때 $T = 300K$ 라 가정하고, $V_T = 26 \cdot 10^{-3} V$.
- $V_D = V_T \cdot \ln \frac{I_x}{I_s}$ 문제에서 $I_s = 2 \times 10^{-15} A$ 라고 주었음.

i) $V_x = 0.5V, 0.8V$ 일 때, $V_{D,ON} = 0.8V$ 은 넘지 못하므로 $I_x = 0, V_{D1} = 0$.

ii) $V_x = 1V$ 일 때.

$$-V_x + I_x R_1 + V_{D1} = 0 \quad V_{D1} = V_x - I_x R_1 = 1 - 2 \times 10^{-15} \cdot \exp\left(\frac{V_{D1}}{26 \cdot 10^{-3}} - 1\right)$$

$$I_x = \frac{1 - V_{D1}}{2000}$$


iii) $V_x = 1.2V$ 일 때 예시.

$$\bullet V_{D1} = 1.2 - 2 \times 10^{-15} \exp\left(\frac{V_{D1}}{26 \cdot 10^{-3}} - 1\right)$$

$$\bullet I_x = \frac{1.2 - V_{D1}}{2000}$$

이 두 식을 풀면 된다.

2.21

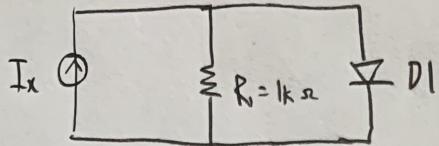


If $I_s = 3 \cdot 10^{-16} A$, calculate V_{D1}
for $I_x = 1mA, 2mA, 3mA$

두 가지 방법이 떠올랐다. 1. $I_x = 1mA, 2mA, 3mA$ 3 가지 경우로 나누어서 $V_D = V_T \cdot \ln \frac{I_x}{I_s}$ 로 V_{D1} 를 구하는 것

2. 전기회로 이론 2에서 배운 Source transformation 을 이용해 R_1 에 걸리는 전압을 통해 V_{D1} 를 구하는 것

첫 번째 방법으로 풀 것이다.

7.

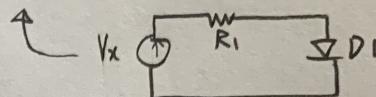

$$i) I_x = 1mA$$

$$V_D = V_T \cdot \ln \frac{I_x}{I_s} = \underbrace{26 \cdot 10^{-3}}_{300K \text{ 일 때}} \cdot \ln \frac{10^{-3}}{\underbrace{3 \cdot 10^{-16}}_{28.8}} = 26 \cdot 10^{-3} \cdot (28.8) = 0.748V$$

$$ii) I_x = 2mA$$


$$V_D = V_T \cdot \ln \frac{I_x}{I_s} = 26 \cdot 10^{-3} \cdot \ln \left(\frac{2}{3} \cdot 10^3 \right) = 26 \cdot 10^{-3} \cdot (29.5) = 0.767V$$

$$iii) I_x = 3mA$$

$$V_D = V_T \cdot \ln \frac{I_x}{I_s} = 26 \cdot 10^{-3} \cdot \ln \left(\frac{4}{3} \cdot 10^3 \right) = 26 \cdot 10^{-3} \cdot (30.22) = 0.785V$$

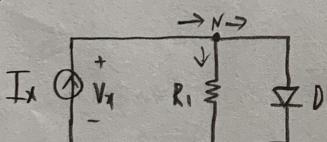2.23

$$I_x = 1mA \rightarrow V_x = 1.2V, I_x = 2mA \rightarrow V_x = 1.8V \text{ 일 때}, R_1, I_s = ?$$



Newton-KCL을 돌려보자.

$$\bullet I_x = \frac{V_x}{R_1} + I_{D1} \quad \dots I_{D1} = I_x - \frac{V_x}{R_1}$$

$$\bullet V_x = V_T \cdot \ln \frac{I_{D1}}{I_s}$$

$$\rightarrow \bullet V_x = V_T \cdot \ln \left(\frac{I_x - \frac{V_x}{R_1}}{I_s} \right)$$

$$I_x = 1mA \text{ 일 때}, 1.2V = 26 \cdot 10^{-3} \cdot \ln \left(1 - \frac{1.2}{R_1} \right) \rightarrow I_s (125.45) = 1 - \frac{1.2}{R_1}$$

$$I_x = 2mA \text{ 일 때}, 1.8V = 26 \cdot 10^{-3} \cdot \ln \left(2 - \frac{1.8}{R_1} \right) \rightarrow I_s (188.18) = 2 - \frac{1.8}{R_1}$$


$$I_s = \frac{1 - \frac{1.2}{R_1}}{125.45} = \frac{2 - \frac{1.8}{R_1}}{188.18}, \frac{188(1 - \frac{1.2}{R_1})}{188(1 - \frac{1.2}{R_1})} = \frac{125(2 - \frac{1.8}{R_1})}{125(2 - \frac{1.8}{R_1})}, 188(R_1 - 1.2) = 125(2R_1 - 1.8)$$

근연성을 위해 소수점 생략


$$(R_1 = 9.67 \times 10^{-5}). I_s =$$

B615065 남재우

2.24.

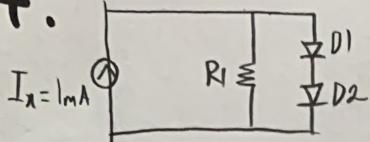

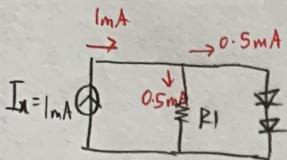determine R_1 such that this resistor carries 0.5 mA. $I_s = 5 \times 10^{-16}$



$$V_x = V_T \cdot \ln\left(\frac{I_D}{I_s}\right)$$

$$= \frac{26}{1000} \cdot \ln\left(\frac{0.5 \text{ mA}}{5 \times 10^{-16}}\right) \\ = \frac{26(27.6310)}{1000} = 0.718$$


R_1 과 다이오드는 parallel 이므로 걸리는 전압 같다.

$$2V_x = 0.5 \text{ mA} \times R_1$$

$$R_1 = 2872 \Omega$$

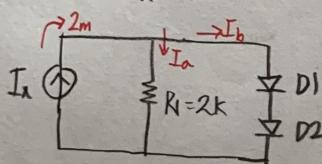2.25

calculate voltage across R_1 for $I_x = 2 \text{ mA}$



$$\bullet I_x = 2 \text{ mA} = I_a + I_b \\ \bullet V_D = V_T \cdot \ln \frac{I_b}{5 \times 10^{-16}}$$

R_1 과 다이오드는 parallel 이므로 걸리는 전압 같다.


$$2k \cdot I_a = 2 \times \frac{2.6}{1000} \times \ln \frac{I_b}{5 \times 10^{-16}}$$

$$2 \times 10^3 (I_a) = 2 \times \frac{2.6}{1000} \times \ln \frac{(2 \cdot 10^{-3} - I_a)}{5 \times 10^{-16}}$$

식을 통배 I_a 를 구하면,


$$V_{R1} = 2000 I_a$$

3.4

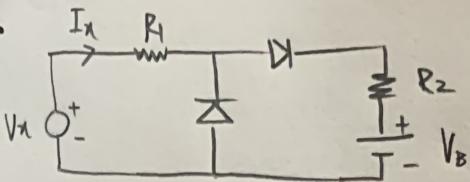

Plot I_x as function of V_x ,
if $V_B = 1V$, $V_B = -1V$.


q). $V_x > 0$.

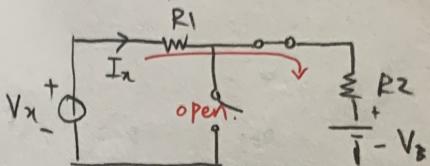


KVL 둘리면,

$$-V_x + I_x R_1 + I_x R_2 = 0. \quad V_B \text{는 추가로 배터리로 따로 추가한다.}$$

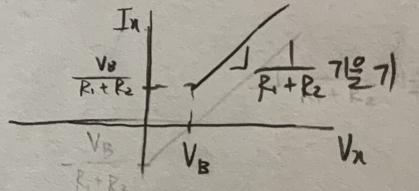
$$I_x(R_1 + R_2) = V_x - V_B \rightarrow I_x = \frac{1}{R_1 + R_2} (V_x - V_B)$$



q). $V_x < 0$ 일 때.

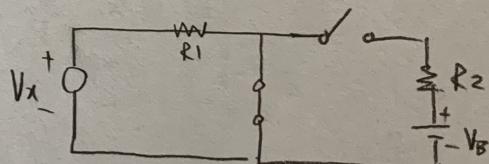


Short 되므로 $\frac{1}{R_1}$ 인 직선이 된다.

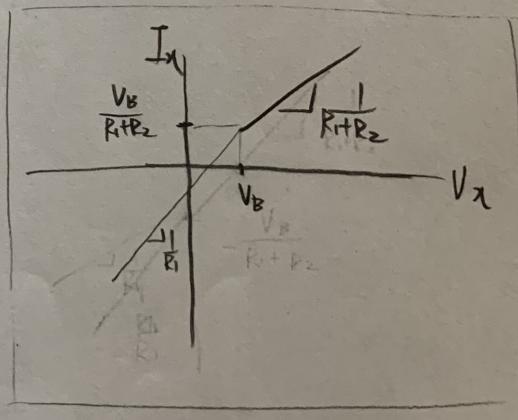

B615065


3.6

Plot I_x as function of V_x , $V_B > 0$

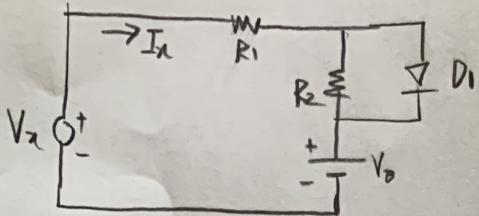

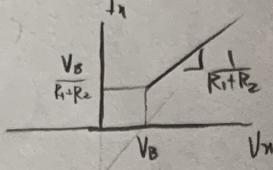
i) $V_x > 0$.

$$-V_x + I_x R_1 + I_x R_2 = 0, \quad V_B \text{는 Plot에 따로} \\ \hookrightarrow I_x = \frac{1}{R_1 + R_2} (V_x - V_B)$$



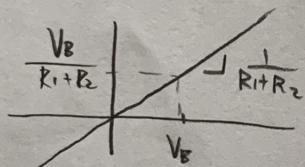
ii) $V_x < 0$.

$$-V_x + I_x R_1 + I_x R_2 = 0 \\ \hookrightarrow I_x = \frac{1}{R_1 + R_2} (V_x)$$




3.11 plot input-output character / ideal model

(a)

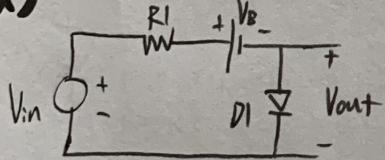


i) $V_{in} > 0$.

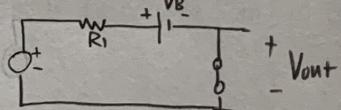


다이오드에 전압이 만 걸리므로, V_{out} 에 걸리는 전압이 없습니다 (V_B 는 배터리로 Plot에 포함)


ii) $V_{in} < 0$.

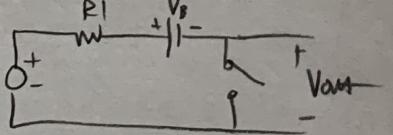


$$V_{in} = V_{out} + V_B$$

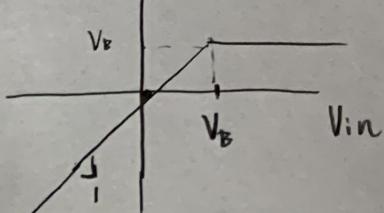

3.11(c)

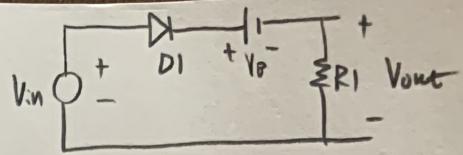


i) $V_{in} > 0$.

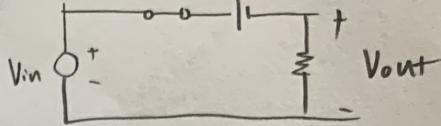


다이오드가 만 걸리므로, R_1 에 걸리는 전압은 V_{in} 과 같게 된다 ($+V_B$)

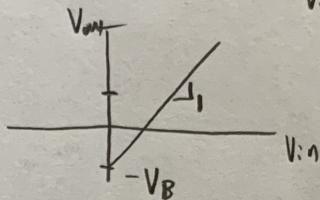
$$\text{KL: } -V_{in} + V_B + V_{out} = 0, \quad V_{in} = V_B + V_{out}$$



ii) $V_{in} < 0$.

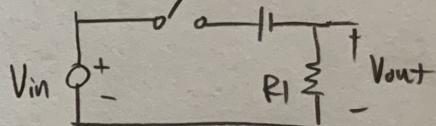


Diode off 만, 전류가 흐르지 않는다.

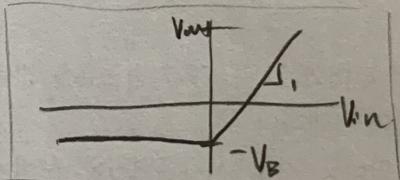

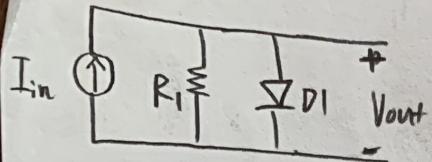
3.14

(a)


Plot current flowing R_1 as function of V_{in} / constant voltage diode model



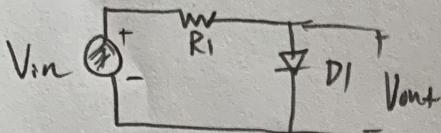전기회로 이론 2에서 배운 Source transformation 을 쓰면




$$i) V_{in} > V_{D,ON}$$

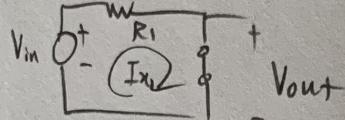


Diode on \rightarrow 전류흐름 \rightarrow R_1 에 전류를 통해 전압降하
VNL로 정확한 수치를 계산하면,

$$-V_{in} + I_x \cdot R_1 + V_{D,ON} = 0$$

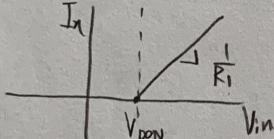
$$I_x = \frac{1}{R_1} (V_{in} - V_{D,ON}) = 0$$



$$ii) V_{in} < V_{D,ON}$$

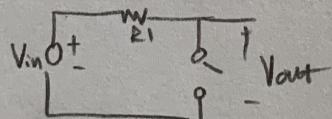


Diode off \rightarrow 전류 X ...

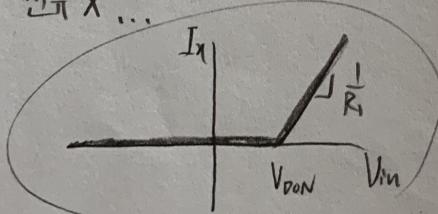


3.19

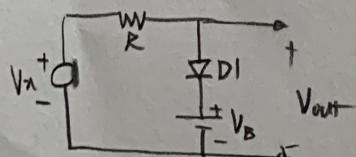(a) Plot input-output 특성 / constant-voltage diode




$$i) V_x > V_{D,ON}$$

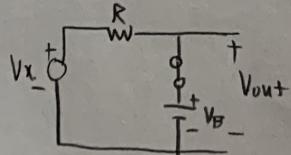

다이오드 on


전류 O \rightarrow 다이오드에 걸리는 전압 = X \rightarrow $V_{out+} = V_B$

$$ii) V_x < V_{D,ON}$$

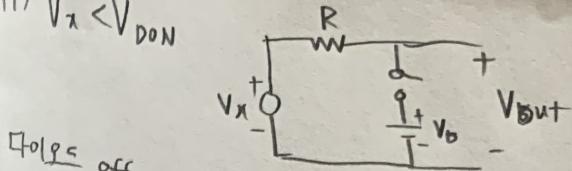

다이오드 off

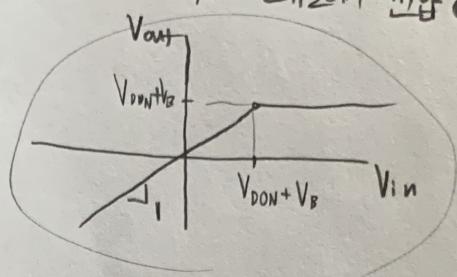R 에 전류보면서 전압 O $\rightarrow V_{out+} = V_x + V_B$




B4505

남재우

4.2

Determine V_{out} / V_{in} .

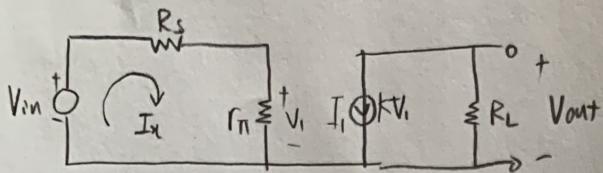

$$\bullet I_x = \frac{V_{in}}{R_s + r_n}$$

$$\bullet +V_{in} + I_x \cdot R_s + V_1 = 0 \rightarrow V_1 = V_{in} - I_x R_s$$

$$\bullet V_{out} = -I_1 R_L = -k V_1 R_L = -k R_L \cdot V_1$$

$$= -k R_L (V_{in} - I_x R_s)$$

$$= -k R_L \left(V_{in} - \frac{R_s}{R_s + r_n} \cdot V_{in} \right)$$

$$V_{out} = V_{in} (-k R_L) \left(\frac{r_n}{R_s + r_n} \right)$$

$$A_v = \frac{V_{out}}{V_{in}} = -k R_L \cdot \frac{r_n}{R_s + r_n}$$

4.5

I_c of Q_2 is twice of Q_1 .

$$V_{BE1} - V_{BE2} = 0.$$

determine ratio of base width.

$$I_{c2} = 2 I_{c1} \leftarrow V_{BE1} = V_{BE2} = V_{BE}$$

각각정.

W_b 의 ratio는?

$$I_{c2} = I_s \exp \frac{V_{BE}}{V_T}$$

other parameters = identical

$$\rightarrow \exp \frac{V_{BE}}{V_T} = \text{same.}$$


$$I_{s2} = 2 I_{s1}$$

$$I_s = \frac{A_E \cdot q \cdot D_n \cdot N_i^2}{N_B \cdot W_B}$$

$2 W_{B2} = W_{B1}$

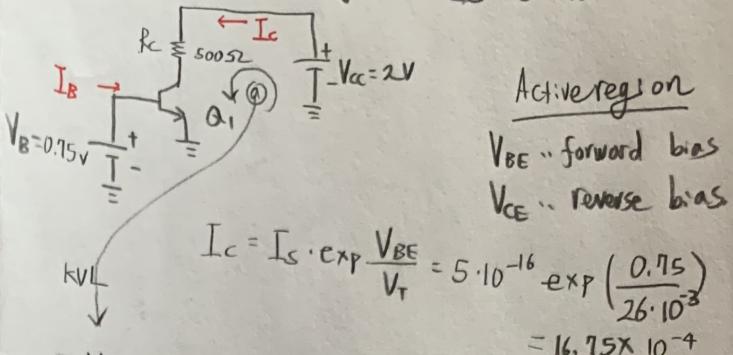4.9

calculate V_{cc} that places Q_1 at edge of active region. $I_s = 5 \times 10^{-16}$.



$$I_c = I_s \cdot \exp \frac{V_{BE}}{V_T} = 5 \cdot 10^{-16} \exp \left(\frac{0.75}{26 \cdot 10^{-3}} \right) = 16.75 \times 10^{-4}$$

$$- V_{cc} + I_c \cdot 1M + V_{Q1} = 0.$$

$$V_{Q1} = V_{cc} - I_c \cdot 1M = V_{cc} - 500 \left(16.75 \right) \frac{1}{10^4} = V_{cc} - 0.8375$$

이3 active region 이 되려면,

$$V_{Q1} \geq V_B (= 0.75) \text{ 이다.}$$

$$V_{cc} - 0.8375 \geq 0.75. \quad V_{cc} \text{는 } 1.5875 \text{ 이상}$$

즉 문제에서처럼 2V일 때, $V_{Q1} = 1.1625V$ 되므로
당연히 active region 이 된다.

4.10

$$I_1 = 1mA, I_2 = 1.5mA, I_s = 3 \cdot 10^{-16} A$$

construct required circuit w/ min number of transistor.


- I_{c1} 에 영향받는 모든 transistor의 I_c 합을 $\sum I_{c1}$ 이라고 가정한다.
- $a = I_1$ 이 영향받는 transistor \neq
- $b = I_2$ \Rightarrow \uparrow 및 가정 한다.

$$\sum I_{c1} = a \times 1 \cdot 10^{-3} = I_s \exp \frac{V_{BE}}{V_T}$$

$$\sum I_{c2} = b \times 1.5 \cdot 10^{-3} = I_s \exp \frac{V_{BE}}{V_T}$$


$$a = 3, b = 2 \Rightarrow \sum I_{c1} = \sum I_{c2} \text{ 이다.}$$

즉,

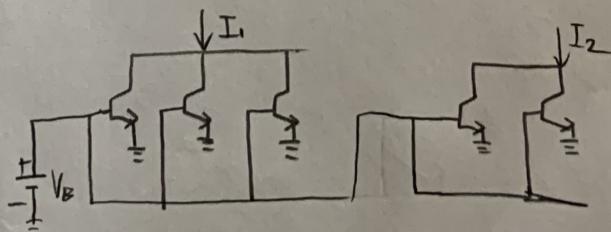

B615065

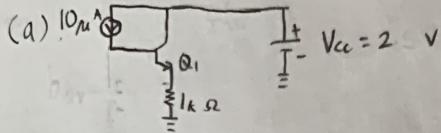4.19 determine operating point and small signal model of Q1
 $I_S = 8 \times 10^{-16} A$, $\beta = 100$, $V_A = \infty$





$$I_B = 10 \cdot 10^{-6} A = 10^{-5} A$$

$$I_C = \beta \cdot I_B = 10^{-3} A$$

$$g_m = \frac{I_C}{V_T} = \frac{10^{-3}}{26 \cdot 10^{-3}} = \frac{1}{26} = 0.038.$$
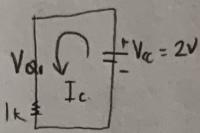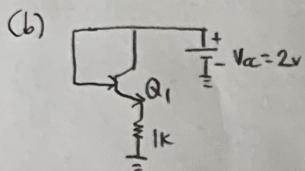
$$r_{\pi} = \frac{\beta}{g_m} = 2631 \Omega$$




$$\text{KVL: } -V_{cc} + V_{Q1} + I_C \cdot R_L = 0$$

$$\rightarrow -2 + V_{Q1} + I_C \cdot 1000 = 0.$$

$$I_C = \frac{1}{1000} (2 - V_{Q1})$$

(c) $I_C R_L = I_E = I_C \cdot 1000$

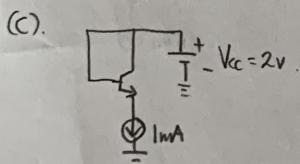

$$I_E = 10^{-3} A$$


$$I_E = \frac{\beta+1}{\beta} I_C = \frac{101}{100} I_C$$

$$I_C = 9.9 \times 10^{-4}$$

$$g_m = \frac{I_C}{V_T} = \frac{9.9 \times 10^{-4}}{26 \cdot 10^{-3}} = 0.038$$

$$r_{\pi} = \frac{\beta}{g_m} = 2631 \Omega$$

4.23

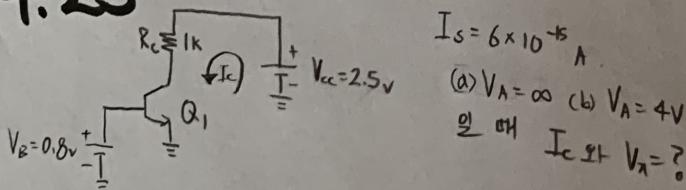

$$I_S = 6 \times 10^{-15} A$$

(a) $V_A = \infty$ (b) $V_A = 4V$
 일 때 I_C 와 $V_A = ?$

1) $V_A = \infty$. Large signal.


KVL
 $I_C = I_S \cdot \exp\left(\frac{V_{BE}}{V_T}\right) = 6 \cdot 10^{-15} \cdot 2.28 \cdot 10^{13} = 0.1368$

 $-V_{cc} + I_C R_C + V_A = 0$
 $-2.5 + 0.1368 + V_A = 0$

$$I_C = 0.1368 A$$

$$V_A = 2.3632 V$$

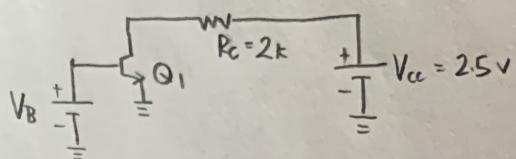4.28 $V_A = \infty$, $I_S = 6 \cdot 10^{-16}$



(a), V_B that Q1 operates at edge of active region.

• $I_C = ?$ 구하자. V_B 도 미지수이므로 I_C 를 이루어진 equation을 개를 찾아보자.

$$\text{NVL} \rightarrow -V_{cc} + I_C \cdot (2k) + V_{Q1} = 0$$

$$\bullet I_C = 6 \cdot 10^{-6} \cdot \exp\left(\frac{V_B}{26 \cdot 10^{-3}}\right) \left(1 + \frac{V_B}{26}\right)$$

$$\bullet V_A = \infty \text{ 일 때}, V_B = V_T \cdot \ln \frac{I_C}{I_S} = 26 \cdot 10^{-3} \cdot \ln \frac{I_C}{6 \cdot 10^{-16}}$$

$$V_{Q1} = 2.5 - 2000 I_C \quad V_B = \frac{26}{1000} \ln \frac{I_C \cdot 10^{16}}{6}$$

$V_{Q1} \geq V_B$.. active region.

$$2.5 - 2000 I_C \geq \frac{26}{1000} \ln \frac{10^{16} I_C}{6}$$

$$\Leftrightarrow \text{만족하는 } I_C = I, V_B = \frac{26}{1000} \ln \frac{I \cdot 10^{16}}{6}$$

(b).

$$V_B = V_T \cdot \ln \frac{200mV}{6 \cdot 10^{-16}} = V_T \cdot \ln \frac{200 \cdot 10^{-3}}{6 \cdot 10^{-16}}$$

$$V_B = V_T \cdot \ln \left(\frac{1}{3} \cdot 10^{19} \right) = (33,44)(V_T)$$

33,44

B615065

남자애